

1 Introduction

1.1 Brief overview

A 4-way traffic controller is designed with four roads labelled as North, East and south and west. The signal go through the sequence North -> East -> South -> West with sequence of light in each road is Green -> Orange -> Red . It basically has six interconnected modules i.e. four Sensor unit (one for each road), one adaptation unit and one display timer unit. The display timer is our control path and the other modules are data paths. The top-level architecture is shown in Figure 1.

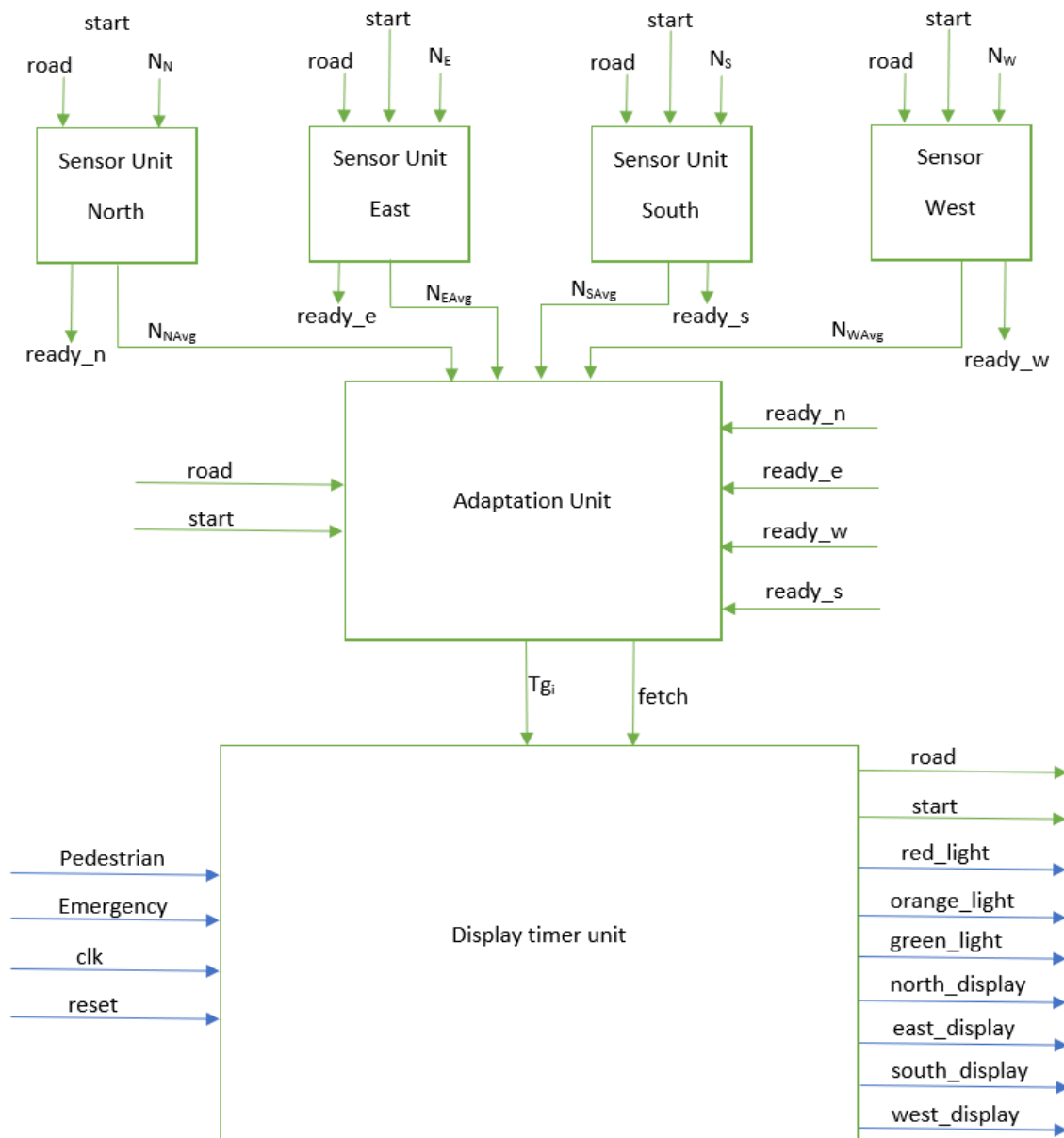


Figure 1: 4-way traffic controller architecture

1.2 Interfaces

The table shown below provides the information about the signals that are shown in Figure 1.

Signal Name	Signal Type	Description																														
Pedestrian	Input	This port will be connected to pedestrian button																														
Emergency	Input	This port will be connected to emergency button																														
clk	Input	This port will be connected to clock input																														
reset	Input	This port will be connected to reset button																														
N_n (N _N)	Input	This is the port that will get number of vehicles in north road from sensor																														
N_e (N _E)	Input	This is the port that will get number of vehicles in east road from sensor																														
N_s (N _S)	Input	This is the port that will get number of vehicles in south road from sensor																														
N_w (N _W)	Input	This is the port that will get number of vehicles in west road from sensor																														
red_light	Output	<div>It is a 4-bit output port containing the status of red light in all four road.</div> <table><tr><th>Condition</th><th>Bit3 (East)</th><th>Bit0 (South)</th><th>Bit1 (East)</th><th>Bit0 (North)</th></tr><tr><td>All red</td><td>1</td><td>1</td><td>1</td><td>1</td></tr><tr><td>All red except North</td><td>1</td><td>1</td><td>1</td><td>0</td></tr><tr><td>All red except East</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>All red except South</td><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>All red except West</td><td>0</td><td>1</td><td>1</td><td>1</td></tr></table>	Condition	Bit3 (East)	Bit0 (South)	Bit1 (East)	Bit0 (North)	All red	1	1	1	1	All red except North	1	1	1	0	All red except East	1	1	0	1	All red except South	1	0	1	1	All red except West	0	1	1	1
Condition	Bit3 (East)	Bit0 (South)	Bit1 (East)	Bit0 (North)																												
All red	1	1	1	1																												
All red except North	1	1	1	0																												
All red except East	1	1	0	1																												
All red except South	1	0	1	1																												
All red except West	0	1	1	1																												
orange_light	Output	<div>It is a 4-bit output port containing the status of orange light in all four road.</div> <table><tr><th>Condition</th><th>Bit3 (East)</th><th>Bit0 (South)</th><th>Bit1 (East)</th><th>Bit0 (North)</th></tr><tr><td>No orange</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>North orange</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>East orange</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>South orange</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>West orange</td><td>1</td><td>0</td><td>0</td><td>0</td></tr></table>	Condition	Bit3 (East)	Bit0 (South)	Bit1 (East)	Bit0 (North)	No orange	0	0	0	0	North orange	0	0	0	1	East orange	0	0	1	0	South orange	0	1	0	1	West orange	1	0	0	0
Condition	Bit3 (East)	Bit0 (South)	Bit1 (East)	Bit0 (North)																												
No orange	0	0	0	0																												
North orange	0	0	0	1																												
East orange	0	0	1	0																												
South orange	0	1	0	1																												
West orange	1	0	0	0																												
green_light	Output	It is a 4-bit output port containing the status of green light in all four road and it's table will look similar to orange_light																														
north_display	Output	It is 12-bit output port for two 7-segment display in north road																														
east_display	Output	It is 12-bit output port for two 7-segment display in east road																														
south_display	Output	It is 12-bit output port for two 7-segment display in south road																														
West_display	Output	It is 12-bit output port for two 7-segment display in west road																														

road	Control signal	It is a used to select the sensor unit of a particular road.	
		Road	Condition
		00	North road sensor is selected
		01	East road sensor is selected
		10	South road sensor is selected
		11	West road sensor is selected
start	Control signal	It is used to start the sensor and adaptation unit	
N_navg (N_{NAvg})	Data signal	It is used to send the average number of vehicles to the adaption unit for north road	
N_navg (N_{EAvg})	Data signal	It is used to send the average number of vehicles to the adaption unit for east road	
N_navg (N_{SAvg})	Data signal	It is used to send the average number of vehicles to the adaption unit for south road	
N_navg (N_{WAv})	Data signal	It is used to send the average number of vehicles to the adaption unit for west road	
ready_n	Data signal	It tells the adaptation unit that the average value is calculated for north road	
ready_e	Data signal	It tells the adaptation unit that the average value is calculated for east road	
ready_w	Data signal	It tells the adaptation unit that the average value is calculated for west road	
ready_s	Data signal	It tells the adaptation unit that the average value is calculated for south road	
T_gi (T_{gi})	Data signal	It send the green time for the selected road to display timer module	
fetch	Data signal	It tells the display timer module that green time for a particular road is calculated.	

2 Functional description

In this section we will discuss all the modules in detailed manner

2.1 Display timer unit

- Under no emergency, pedestrian and reset signal, display timer unit will cycle from state S0 to S7 and then back to S0. State is changed when the time for the current state is over.
- When emergency signal is given between any green signal, then that state will be changed followed by the orange light in that same road and after that all the light will go red for 10 second and then the system will go to the state next to the state just before the all red state.
- When pedestrian signal is pressed between any orange signal, then all lights red will go red after the time for current orange light is over and all red state will be active for only 10 seconds and after that the system will go to the state next to state just before the all red state.
- When the reset is pressed then all the lights will go red instantly and it will stay red for 10 seconds and after that the system will start the normal function from S0 state. This same condition is also our all red condition
- There are four different counter used for denoting the time of the lights for each road

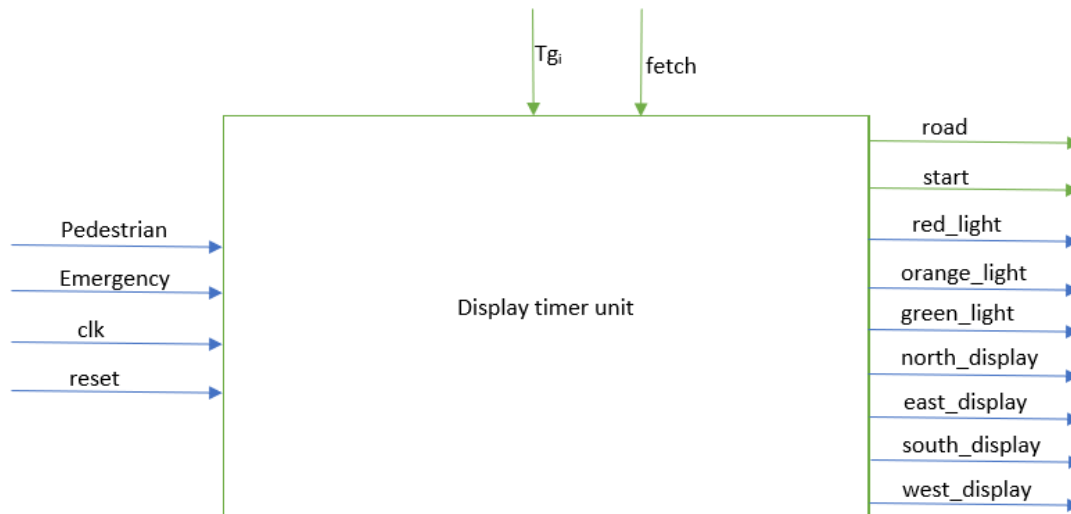


Figure 2: Block diagram of display timer unit

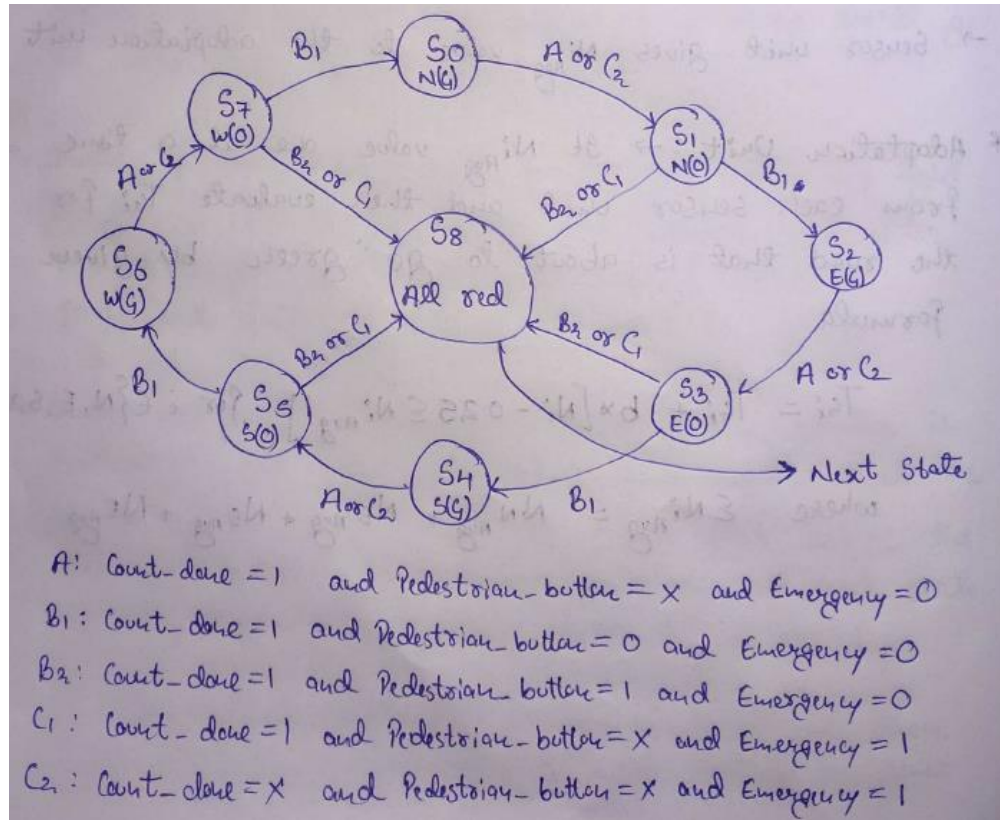


Figure 3: FSM of Display timer unit

State Table:

State	Value	Description
S0	0000	Represent North green
S1	0001	Represent North orange
S2	0010	Represent East green
S3	0011	Represent East orange
S4	0100	Represent South green
S5	0101	Represent South orange
S6	0110	Represent West green
S7	0111	Represent West orange
S8	1000	Represent All red condition

Module used in this unit:

1. **Clock Divider module:** This module is used to lower the frequency of input clock which is assumed to be 100MHz and brought down to 1Hz with the help of this module so that it is easier to create the delay having the magnitudes in seconds for the light and 7-segment display.

```

module clock_divider(clk,divided_clk);
input wire clk; //100Mhz
output reg divided_clk = 0; //1Hz
localparam count_value=49999999;
integer count=0;

always @(posedge clk)
begin
if (count==count_value)
begin
count<=0;
divided_clk<=~divided_clk;
end
else
begin
count<=count+1;
divided_clk<=divided_clk;
end
end
endmodule

```

Figure 4: Clock divider module

2. **Binary to BCD module:** This module is used to convert the countdown for lights of each road to BCD value from a binary value so that it can be easily decoded for a seven segment display.

```

module binary_to_bcd(bcd_out,binary_in);
input [7:0] binary_in;
output reg [11:0] bcd_out;
reg [3:0] i;

always @(binary_in)
begin
bcd_out=0;
for(i=0;i<8;i=i+1)
begin
bcd_out={bcd_out[10:0],binary_in[7-i]};

if(i<7 && bcd_out[3:0]>4)
bcd_out[3:0]=bcd_out[3:0]+3;
if(i<7 && bcd_out[7:4]>4)
bcd_out[7:4]=bcd_out[7:4]+3;
if(i<7 && bcd_out[11:8]>4)
bcd_out[11:8]=bcd_out[11:8]+3;
end
end
endmodule

```

Figure 5: Binary to BCD module

3. **BCD to 7-segment module:** This module is used to display the count in 7-segment display of each road from the equivalent BCD value of the count corresponding to that road.

```
module bcd_to_7segment(display_out,bcd_in,clk);  
    input clk;  
    input [3:0] bcd_in;  
    output reg [6:0] display_out; //abdefg  
  
    always @(posedge clk)  
    begin  
        case(bcd_in)  
            4'b0000: display_out = 7'b1111110;  
            4'b0001: display_out = 7'b0110000;  
            4'b0010: display_out = 7'b1101101;  
            4'b0011: display_out = 7'b1111001;  
            4'b0100: display_out = 7'b0110011;  
            4'b0101: display_out = 7'b1011011;  
            4'b0110: display_out = 7'b1011111;  
            4'b0111: display_out = 7'b1110000;  
            4'b1000: display_out = 7'b1111111;  
            4'b1001: display_out = 7'b1111011;  
            default: display_out = 7'b1111110;  
        endcase  
    end  
endmodule
```

Figure 6: BCD to 7-segment module

3 Testbench

```
Project Summary x display_timer.v x bcd_to_7segment.v x binary_to_bcd.v x test_bench.v x
C:/Users/preea/OneDrive/Documents/Vivado/Traffic_light_controller/Traffic_light_controller.srcs/sim_1/new/test_bench.v

17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22
23 module test_bench();
24 reg clk,reset,emg,ped;
25 wire [3:0] red, orange, green;
26 wire [11:0] display_north,display_east,display_south,display_west;
27
28 display_timer abc(red,orange,green,display_north,display_east,display_south,display_west,ped,emg,clk,reset);
29
30 initial
31 begin
32 clk=1'b0;
33 reset=1'b0;
34 emg=0;
35 ped=0;
36 #150 reset=1'b1;
37 #1 reset=1'b0;
38 #14 emg=1'b1;
39 #1 emg=1'b0;
40 #112 ped=1'b1;
41 #1 ped=1'b0;
42 #200 $finish;
43
44 end
45
46 always #0.5 clk=~clk;
47 endmodule
48
```



4 Bugs known at submission date

- Time adaptation part of the display timer unit is not been executed as it was not properly implemented and hence the timing for lights are already defined in the code and it stays same throughout the simulation
- Clock Divider module is working properly (checked separately) but it is still not used while simulation because the simulation becomes too slow when we clock divider is used but still it can be implement at the end when all the things are perfect.